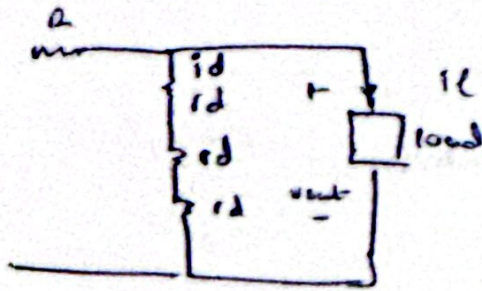


(101)

circuit can be simplified as:



$$r_d = \frac{V_T}{I_D} = \frac{26 \text{ mV}}{5 \text{ mA}} = 5.2 \Omega \quad \text{from eq 3-60}$$

$$\text{Since } i_L = +1 \text{ mA}$$

$$i_d = -1 \text{ mA}$$

$$\begin{aligned} \text{change in } v_{out} &= (-1 \text{ mA}) (2 \times 5.2) \\ &= -10.4 \text{ mV} \end{aligned}$$

(12)

$$V_R \approx \frac{1}{2} \frac{V_p - 5V_{oon}}{R_1 C_1 f_{in}}$$

$$V_p = 5 \text{ volts}$$

$$R_L = 1 \text{ k}\Omega$$

$$C_1 = 100 \mu\text{F}$$

$$f_{in} = 50 \text{ Hz}$$

Plug in the values.

$$\frac{1}{2} \frac{5 - 5(0.8)}{1000 \times 100 \times 10^{-6} \times 50}$$

$$= 150 \text{ mV or } 0.15 \text{ volts. } 100 \text{ mV or } 0.1 \text{ volts.}$$

(b) The bias current through the diodes is the same as the bias current through  $R_1$ .

$$\frac{V_p - 5(0.8)}{R_1} = 1 \text{ mA}$$


$$r_d = \frac{V_T}{I_D} = 26 \Omega$$

$$V_{R_{load}} = \frac{3rd}{R_1 + 3rd} V_R = \cancel{V_p - 126 \Omega \text{ bias}}$$

$$V_{R_{load}} = 7.23 \times 10^{-3}$$



(Q3)

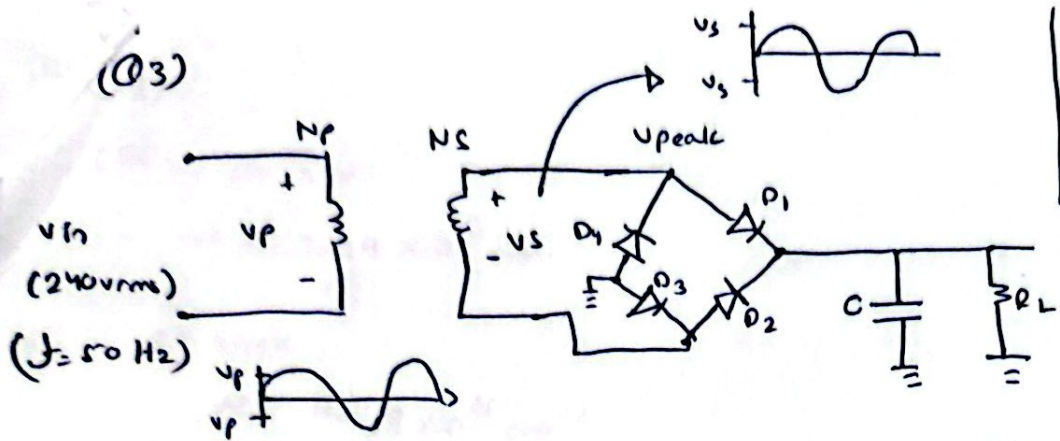

Note:  $150 \Omega$  used  
Same calculation but with  $100 \Omega$   
should be done

$$v_{out} = v_{dc} = 15V$$

$$R_L = 150 \Omega$$

$$\text{ripple} = 1\%$$

$$I_{dc} = \frac{v_{dc}}{R_L} = \frac{15}{150} = 0.1A$$

Diode:

$$Avg\ peak = v_{dc} / 150 \Omega = 100mA$$

$$= v_{peak} / 150 \Omega = 157.1mA$$

Capacitor:

$$VR \geq 1\% \text{ of } v_{dc} = 0.15V$$

$$VR = \frac{I_L}{2fC} \Rightarrow C = \frac{I_L}{2VRf}$$

$$C \geq 6.667mF$$

$$\text{we know that } v_{dc} = \frac{2}{\pi} v_{peak} \text{ (or } I_{dc} = \frac{2}{\pi} I_{peak})$$

$$I_{peak} = \frac{\pi}{2} I_{dc} = \frac{\pi}{2} (0.1) = 0.1571A$$

$$v_{peak} = \frac{\pi}{2} v_{dc} = \frac{\pi}{2} (15) = 23.565V$$

two diodes in the complete path results in voltage drop across two diodes i.e.,  $v_{diode} = 2 \times 0.7 = 1.4V$  drop

$$v_{peak} = v_{peak} + v_{diode} = 23.565 + 1.4 =$$

$$v_{peak} = 24.965V = v_s \text{ (voltage at secondary transformer)}$$

$$v_p = 240V_{rms}$$

$$v_p = \sqrt{2} \times 240 \text{ (peak)}$$

$$v_p = 339.411V$$

Turn ratio

$$\frac{N_p}{N_s} = \frac{v_p}{v_s} = \frac{339.411}{24.965} = N_p : N_s = 13.6:1 \text{ (step down)}$$

PIV rating = 1.5 to 2 times  $v_{peak} =$

$$2 \times 24.965 = 49.93 \approx 50V$$

$I_{dc(max)}$  rating = 1.5 to 2 times  $I_{peak}$

$$2 \times \frac{24.965}{150} = 0.1664 \approx 0.1667A$$

Q4)

(a)

At 300K

$$n_i = 2.049 \times 10^{13} \text{ cm}^{-3}$$

for Si

$$n_i \text{ at } 300\text{K} = 1.078 \times 10^{10} \text{ cm}^{-3}$$

At 600K

$$n_i = 4.0149 \times 10^{16} \text{ cm}^{-3}$$

$$n_i \text{ at } 600\text{K} = 1.526 \times 10^{15} \text{ cm}^{-3}$$

The intrinsic carriers are more in Ge than Si for both temperatures 300K and 600K.

(b)

$$n = N_D = 5 \times 10^{16} \text{ cm}^{-3}$$

at  $T = 300\text{K}$

$$n_i^2 = np$$

$$p = \frac{n_i^2}{N_D} = 1.25 \times 10^{10} \text{ cm}^{-3}$$

at  $T = 600\text{K}$

$$n_i^2 = np$$

$$p = \frac{n_i^2}{N_D} = 3.442 \times 10^{16} \text{ cm}^{-3}$$

(05)

electrons

a) Mobility in Silicon =  $1350 \text{ cm}^2/\text{V}\cdot\text{s}$

Mobility of holes in Si =  $480 \text{ cm}^2/\text{V}\cdot\text{s}$

$$E_{\text{field}} = 0.1 \frac{\text{V}}{\mu\text{m}}$$

$$\begin{aligned} \text{velocity of electrons} &= \mu_n E = \left(1350 \frac{\text{cm}^2}{\text{V}\cdot\text{s}}\right) \left(0.1 \frac{\text{V}}{\mu\text{m}}\right) \\ &= 1.35 \times 10^4 \text{ m/s} \end{aligned}$$

$$\begin{aligned} \text{velocity of holes} &= \mu_p E = \left(480 \frac{\text{cm}^2}{\text{V}\cdot\text{s}}\right) \cdot \left(0.1 \frac{\text{V}}{\mu\text{m}}\right) \\ &= 4.8 \times 10^3 \text{ m/s} \end{aligned}$$

(b)

$E = 0.1 \text{ V}/\mu\text{m}$  hole current is negligible as stated

$\mu_n = 1350 \text{ cm}^2/\text{V}\cdot\text{s}$        $\mu_p = 480 \text{ cm}^2/\text{V}\cdot\text{s}$

$$J_{\text{tot}} = 1 \text{ mA}/\mu\text{m}^2 = q [\mu_n n E + 0] \quad \begin{matrix} \nearrow \text{negligible} \\ \end{matrix} = q \mu_n n E$$

$$\begin{aligned} n &= \frac{J_{\text{tot}}}{q \mu_n n E} = \frac{1 \text{ mA}/\mu\text{m}^2}{(1.6 \times 10^{-19}) (1350 \text{ cm}^2/\text{V}\cdot\text{s}) (0.1 \text{ V}/\mu\text{m})} \\ &= 4.6 \times 10^{17} \text{ cm}^{-3} \end{aligned}$$



06)

$$L = 0.1 \mu\text{m} \quad A = (0.05 \mu\text{m})^2 \quad V = 1 \text{V}$$

$$\mu_n = 1350 \text{ cm}^2/\text{Vs} \quad \mu_p = 480 \text{ cm}^2/\text{Vs}$$

$$n = 10^{17} \text{ cm}^{-3}$$

(a)

$$n_i(T=300\text{K}) = 5.2 \times 10^{15} (300)^{3/2} \exp \left[ \frac{-1.12 \text{ eV}}{2(1.38 \times 10^{-23}) \times (300)} \right]$$

$$= 1.077 \times 10^{10}$$

$$= 1.08 \times 10^{10} \text{ cm}^{-3}$$

$$\rho = \frac{n_i^2}{n} = 1.17 \times 10^3 \text{ cm}^{-3} \quad E = V/L = 10 \text{ V}/\mu\text{m}$$

$$I_{\text{tot}} = A \cdot J_{\text{tot}} = A \cdot q [ \mu_n n + \mu_p \rho ] E$$

$$= A \cdot q [ \mu_n n + \mu_p (n_i^2/n) ] E$$

$$10 (\text{V}/\mu\text{m}) \times (0.05 \mu\text{m})^2 (1.6 \times 10^{-19}) \left[ \frac{1350 \text{ cm}^2}{\text{Vs}} (10^{17} \text{ cm}^{-3}) + \right.$$

$$\left. \frac{480 \text{ cm}^2}{\text{Vs}} (1.17 \times 10^3 \text{ cm}^{-3}) \right]$$

$$\times 10 (\text{V}/\mu\text{m})$$

$$I_{\text{tot}} = 0.054 \text{ mA}$$

b)  $400\text{K}$ ,  $n_i = 3.7 \times 10^{12} \text{ cm}^{-3}$ ,  $\rho = n_i^2/n = 1.4 \times 10^8 \text{ cm}^{-3}$ ,  $E = 10 \text{ V}/\mu\text{m}$

$$I_{\text{tot}} = A \cdot q [ \mu_n n + \mu_p (n_i^2/n) ] E$$

$$(10 \text{ V}/\mu\text{m}) \times (0.05 \mu\text{m})^2 \times 1.6 \times 10^{-19} \left[ \frac{1350 \text{ cm}^2}{\text{Vs}} (10^{17} \text{ cm}^{-3}) + \frac{480 \text{ cm}^2}{\text{Vs}} (1.4 \times 10^8 \text{ cm}^{-3}) \right]$$

$$I_{\text{tot}} = 0.054 \text{ mA}$$

(Q7)

$$N_D = 3 \times 10^{16} \quad n_i = 1.08 \times 10^{10} \text{ cm}^{-3}$$

$$V_0 = ?$$

$$V_0 = \frac{kT}{q} \ln \left( \frac{N_D N_A}{n_i^2} \right) = \frac{kT}{q} \ln \left( \frac{N_D}{n_i} \right)$$

$$= \frac{(1.38 \times 10^{-23} \text{ J/K})(300)}{1.6 \times 10^{-19}} \ln \left( \frac{3 \times 10^{16} \text{ cm}^{-3}}{1.08 \times 10^{10} \text{ cm}^{-3}} \right)$$

$$= 0.384 \text{ volts.}$$

(Q8)

$$\frac{C_{j0}}{\sqrt{1 + \frac{0.5}{V_0}}} = 2.2 \rightarrow \text{eq 1}$$

$$\frac{C_{j0}}{\sqrt{1 + \frac{1.5}{V_0}}} \rightarrow \text{eq 2}$$

$$1 \div 2 = \frac{1 + 1.5/V_0}{1 + 0.5/V_0} = \left( \frac{2.2}{1.3} \right)^2 = V_0 = 0.0365 \text{ V}$$

↳ put in eq 1

$$C_{j0} = 2.2 \times \sqrt{1 + \frac{0.5}{V_0}} = 8.43 \text{ fF } / \mu\text{m}^2$$

$$\frac{N_A N_D}{N_A + N_D} = (C_{j0})^2 \cdot V_0 \cdot \frac{2}{\epsilon_{Si}}$$

$$= \left( 8.43 \frac{\text{fF}}{\mu\text{m}^2} \right)^2 \times (0.0365 \text{ V}) \cdot \frac{2}{\epsilon_{Si}} \approx 3.13 \times 10^{17} \text{ cm}^{-3}$$

$$N_A > \frac{N_A N_D}{N_A + N_D} \approx y \quad [\text{trying a value for } N_A]$$

$$N_A = 2 \times 10^{16} \text{ cm}^{-3} \Rightarrow N_D = \frac{y N_A}{N_A - y} = \frac{(3.13 \times 10^{17} \text{ cm}^{-3})(2 \times 10^{16} \text{ cm}^{-3})}{(2 \times 10^{16} - 3.13 \times 10^{17}) \text{ cm}^{-3}}$$
$$\approx 3.71 \times 10^{17} \text{ cm}^{-3}$$



9)

(a) In forward bias,  $I_D = 1 \text{ mA}$ ,  $V_D = 750 \text{ mV}$

$$\therefore I_S \approx I_{D0} e^{-V_D/V_T} = (1 \text{ mA}) (\exp) [-750 \text{ mV} / 26 \text{ mV}]$$

$$= 2.97 \times 10^{-16} \text{ A}$$


b) Since  $I_S \propto \text{Area}$ , doubling area implies doubling  $I_S$  from a

$$I_D = 1 \text{ mA} = 2 \times I_S e^{V_D/V_T}$$

$$V_D = V_T \ln \left( \frac{I_D}{2 I_S} \right) = (26 \text{ mV}) \ln \left( \frac{1 \text{ mA}}{2.297 \times 10^{-16} \text{ A}} \right)$$

$$= 0.732 \text{ volts}$$

(b)

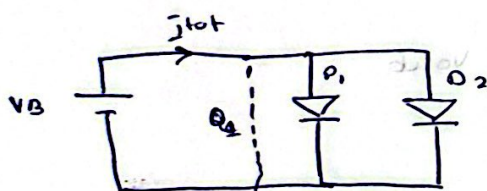

$$I_{tot} = I_{D1} + I_{D2} = I_{S1} (e^{V_B/V_T} - 1) + I_{S2} (e^{V_B/V_T} - 1)$$

$$I_{tot} = (I_{S1} + I_{S2}) (e^{V_B/V_T} - 1)$$

Therefore the parallel combination operates as an exponential device, with an equivalent saturation current  $= I_{S1} + I_{S2}$

By KVL  $V_{D1} = V_{D2}$

$$V_T \ln \left( \frac{I_{D1}}{I_{S1}} \right) = V_T \ln \left( \frac{I_{D2}}{I_{S2}} \right)$$

Also,  $I_{tot} = I_{D1} + I_{D2} \Rightarrow I_{D2} = I_{tot} - I_{D1}$



$$\therefore v_T \ln \left( \frac{I_{O1}}{I_{S1}} \right) = v_T \ln \left( \frac{I_{tot} - I_{O1}}{I_{S2}} \right)$$

$$I_{O1} = I_{tot} \left( \frac{I_{S1}}{I_{S1} + I_{S2}} \right)$$


$$I_{O2} = I_{tot} \left( \frac{I_{S2}}{I_{S1} + I_{S2}} \right)$$

(Q10)

for a half wave rectifier:


- it allows only one half cycle of AC input to pass. When the negative cycle of AC input happens, the diode is reversed biased and the entire AC voltage (peak voltage) appears across the diode.

$$PIV = V_p$$

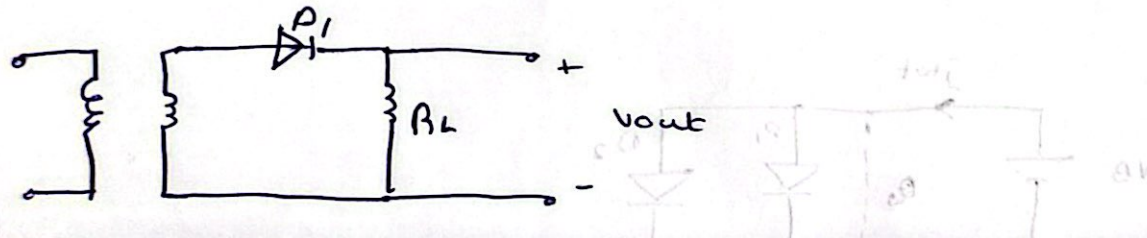


(c)(b)

PIV (full wave bridge rectifier)

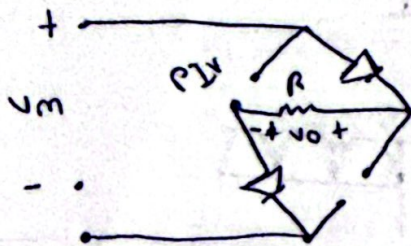

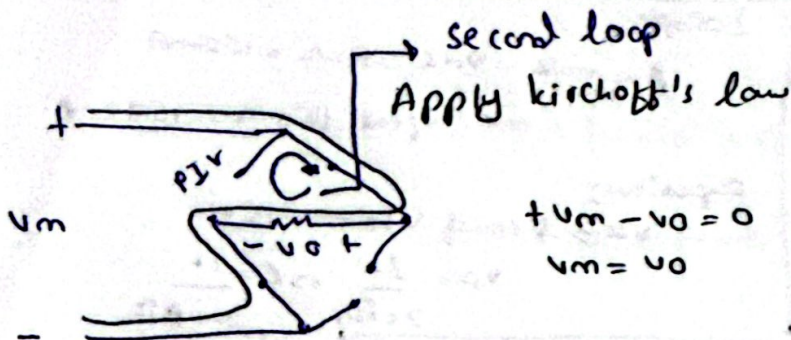diodes will be treated as short circuit  
replace diodes with 



second loop  
Apply kirchoff's law

$$+V_m - V_o = 0$$
$$V_m = V_o$$



Apply kirchoff's law denoted by the arrow.

$$-V_o + PIV = 0$$

$$-V_m + PIV = 0$$

$PIV = V_m$  hence proved.

PIV (full wave center tapped circuit).

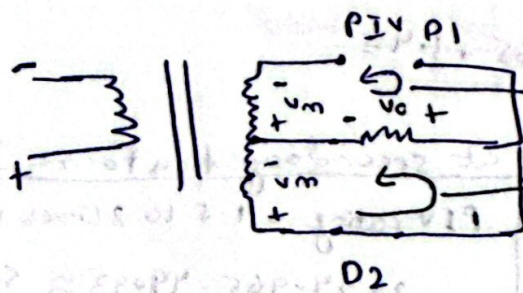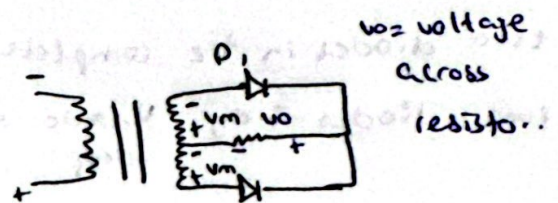

Apply kirchoff in this loop next

Apply kirchoff's in this loop.

$$+V_m - V_o = 0$$

$$V_m = V_o$$

$$+V_o - PIV + V_m = 0$$

$$V_m - PIV + V_m = 0$$

$$2V_m = 2PIV$$