

Lab 08

MOSFET Characteristics

Name: Syed M. Asad Ali Hiba Aiman Ali, M. Asad Siddiqui

Student ID: sa09475, ha09269, ms09200

8.1 Objective

To investigate the characteristics of MOSFET (Metal Oxide Semiconductor Field Effect Transistor) through its characteristic curves

8.2 Introduction to MOSFETs

MOSFETs (Metal-Oxide-Semiconductor Field-Effect Transistors) are the type of FETs (field-effect transistors) in which the metal gate electrode is separated from the semiconductor by an insulator and therefore, also known as Insulated Gate Field Effect Transistors (IGFET). Unlike the current-controlled bipolar device (BJT), which requires base current to allow the current to flow in the collector, the MOSFET device is a **voltage-controlled** unipolar device because the conduction is controlled by voltage and it uses only the majority carriers in conduction. MOSFETs surpass all other devices in switching speed, where switching speeds can exceed a few megahertz. MOSFETs can be mainly categorized as enhancement type and depletion type.

8.3. Pre-Lab Task

Task 1:


- i. Mention various types of MOSFET and applications of MOS.
- ii. Construct complete structure of Enhancement and Depletion type MOSFETs

Part (i):

Types of MOSFETs: E-MOSFETs, D-MOSFETs, N-Channel MOSFET, P-Channel MOSFET, CMOS, Power MOSFET, Vertical MOSFET, FinFET, TFET.

Applications: Digital Electronics, Power Electronics, Analog Circuits, RF and Communication Systems, Automotive Industry and Medical Electronics.

Part (ii):

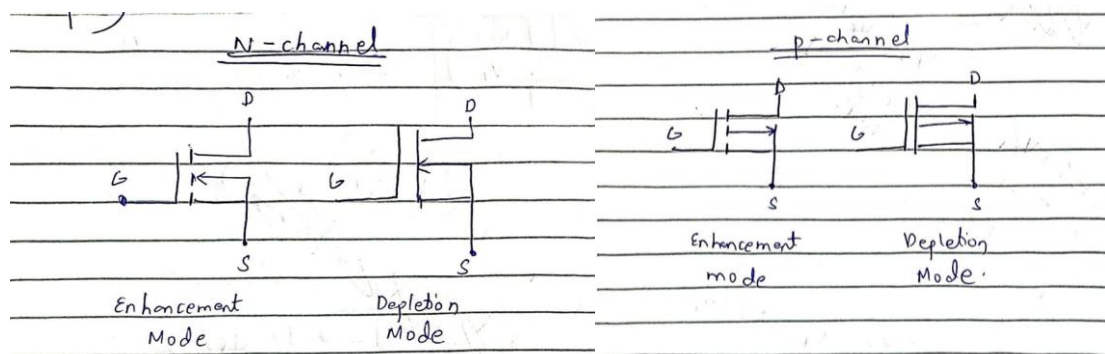

8.4. Structure

The basic structure of MOSFET is shown in Figure 1. The structure consists of three layers: the metal gate electrode, the insulating oxide layer (SiO_2) and the bulk semiconductor. It is an enhancement type n-channel MOSFET. It consists of a lightly doped p-type substrate in which two heavily doped n-regions are formed at the two ends by the process of diffusion. The n-channel and p-channel enhancement type MOSFETs are represented by the symbols given in Figure 1 (b) and (c). It has three terminals; drain (D), gate (G) and source (S). The body (also called substrate) and source are internally short.

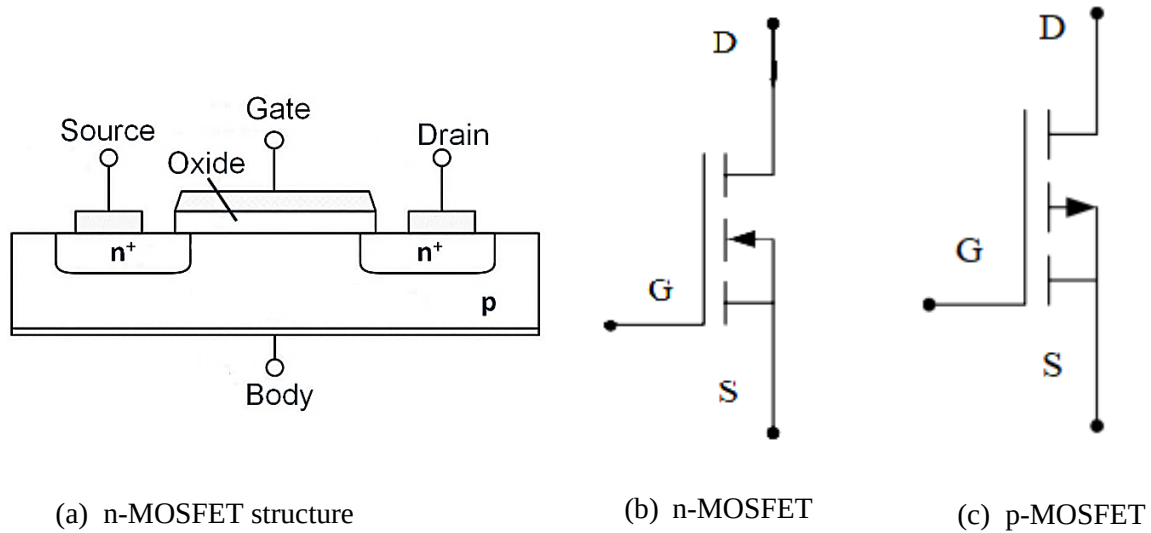


Figure 1: Structure and symbol of MOSFET

9. Regions of Operation

Initially for the enhancement type MOSFETs, the channel between the source and drain terminals required for flow of current is non-existent. This channel is created or “enhanced” by the minority charge carriers of the substrate under the influence of field created by the voltage applied gate terminal V_G when it reaches a certain threshold called threshold voltage V_{th} . Now, if voltage is applied between drain and source terminals V_{DS} , flow of current starts through the channel. This current I_D increases linearly as V_{DS} is increased before saturation occurs. At saturation, the phenomenon of channel pinch-off starts and after that if V_{DS} is further increased, the current I_D becomes almost constant. Therefore, the MOSFET operates in the following three regions given in Table 1.

Table 1: Regions of operation of MOSFET

Region of Operation	Condition	Description
Cut-off Region	n-channel: $V_{GS} < V_{th}$ p-channel: $V_{GS} > V_{th}$	The device operates in off-state since channel is not induced.
Triode Region	n-channel: $V_{DS} < V_{GS} - V_{th}$ and $V_{GS} \geq V_{th}$ p-channel: $V_{DS} > V_{GS} - V_{th}$ and $V_{GS} \leq V_{th}$	The channel is continuous with no pinch-off, resulting in drain current proportional to the channel resistance.
Saturation Region	n-channel: $V_{DS} > V_{GS} - V_{th}$ and $V_{GS} \geq V_{th}$ p-channel: $V_{DS} < V_{GS} - V_{th}$ and $V_{GS} \leq V_{th}$	The channel pinches off resulting in constant drain current.

In this lab, we will investigate the characteristics of the 2N7000 n-channel enhancement type MOSFET. The datasheet can be accessed using this [link](#).

Task 2: To determine the threshold voltage of MOSFET 2N7000

1. Implement the circuit shown in Figure 2 using the 2N7000/Design Cache MOSFET model in PSpice. Model number 2N7000/NPX MOSFET


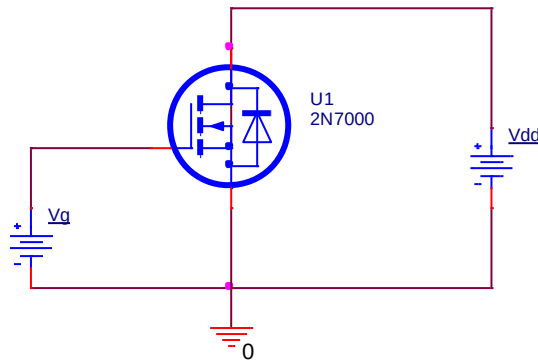


Figure 2: Voltage applied at drain and gate terminals of 2N7000 MOSFET


2. To determine the threshold voltage of MOSFET, first we apply fixed voltage across drain the to source terminal and then gradually increase the gate voltage. The gate to source voltage at which current starts flowing from drain to source will be threshold voltage V_{th} .
3. Set V_{dd} at 10V. Perform DC sweep to vary the voltage of source connected at the gate terminal from 0 to 5 V in steps of 0.01V. In other words, V_g is the primary sweep variable.
4. Obtain plot of drain current I_D as a function of V_{GS} . Determine the threshold voltage i.e. the voltage after which conduction starts. Add capture of the obtained plot.

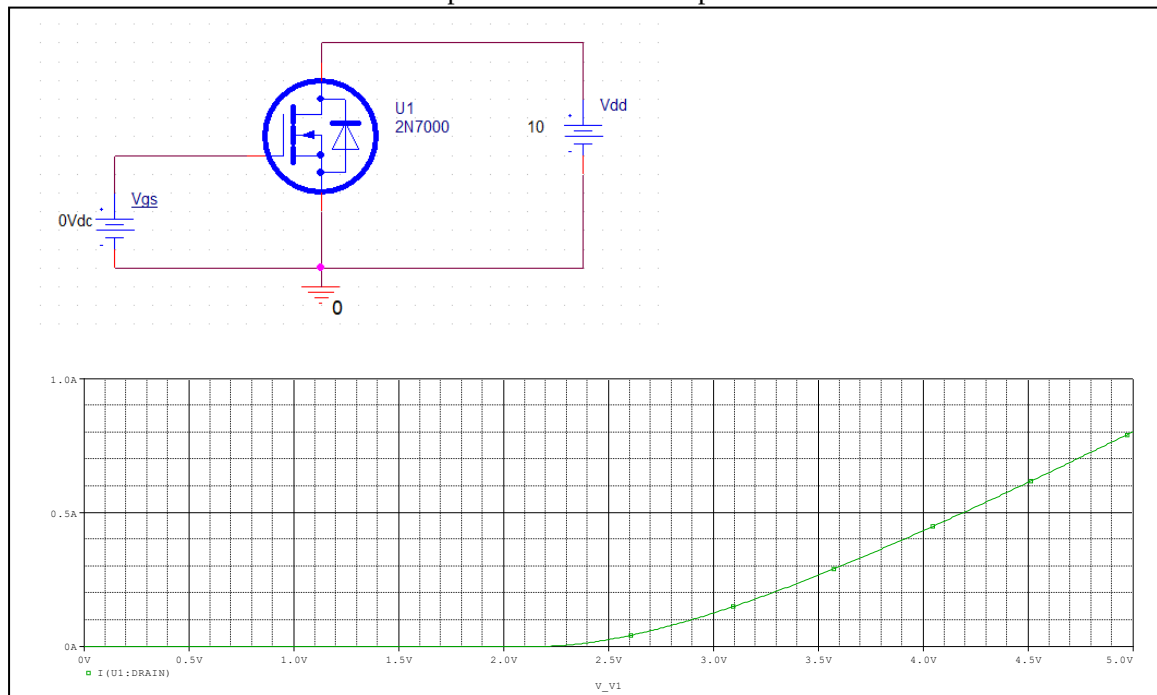

Task 3: To obtain the drain characteristic curve of MOSFET 2N7000

Drain characteristic curve of MOSFET is a plot of the drain current as a function of drain-source voltage for given gate-source voltage.


1. Create a new simulation profile. For the circuit shown in Figure 2, now set V_{GS} equal to 3V and sweep the drain-to-source voltage from 0 to 10V in step size of 0.01.
2. Obtain drain characteristic curve and mention the gate-to-source voltage for which the curve is obtained.
3. Keeping in mind the determined threshold voltage from Task 1 and the conditions given in Table 1, determine the modes of operation of MOSFET and add text labels on the plot. By putting value of threshold voltage and applied gate voltage, show which condition is satisfied in which region.

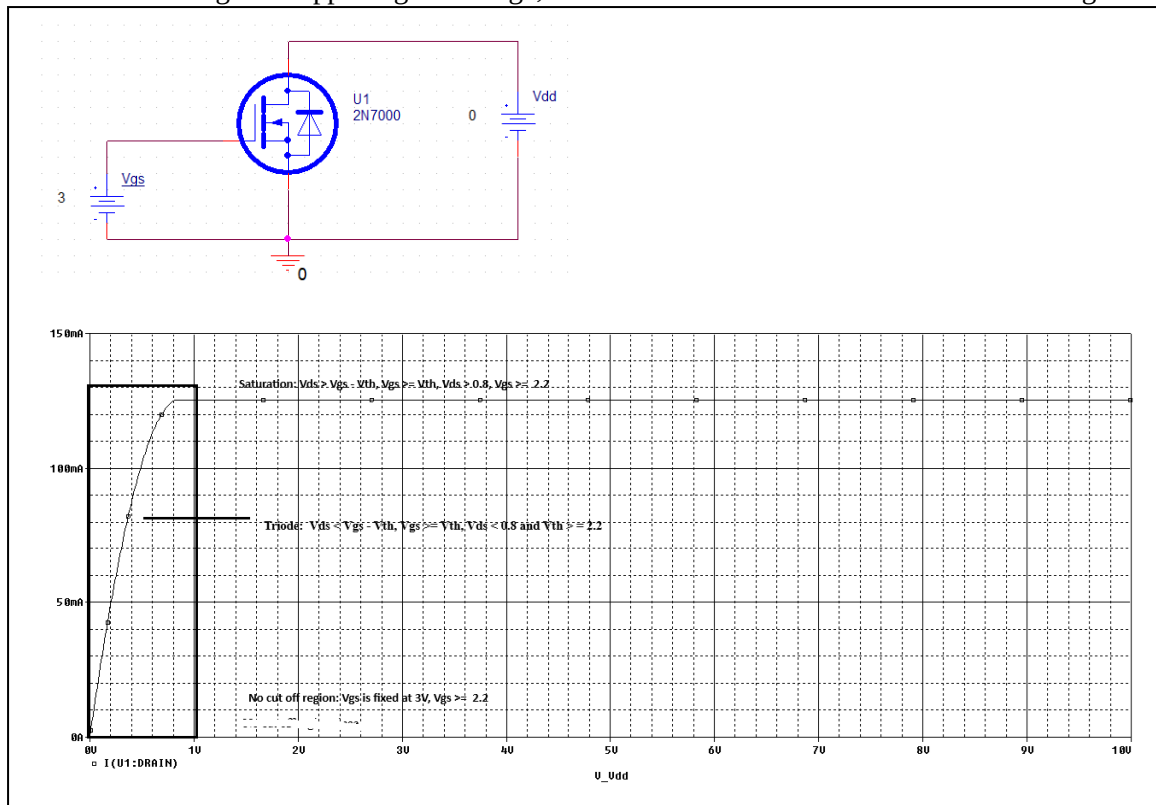

Task 4: To investigate the effect of gate voltage on the drain characteristics of MOSFET 2N7000

To investigate the effect of gate-to-source voltage, one can obtain drain characteristic curves for different values of gate-to-source voltage.

1. Modify the DC Sweep Analysis settings to include secondary sweep for gate-to-source voltage. The gate-to-source voltage is to be varied from 2 to 5V in steps of 1V.
2. Obtain drain current curve as a function of drain-to-source voltage. It should show a different curve for each gate voltage.
3. Identify and mention corresponding V_{GS} for each curve. Also, mention the cut-off region here. Add capture of the plot.
4. Analyze the impact of gate-to-source voltage on the curves and drain current.

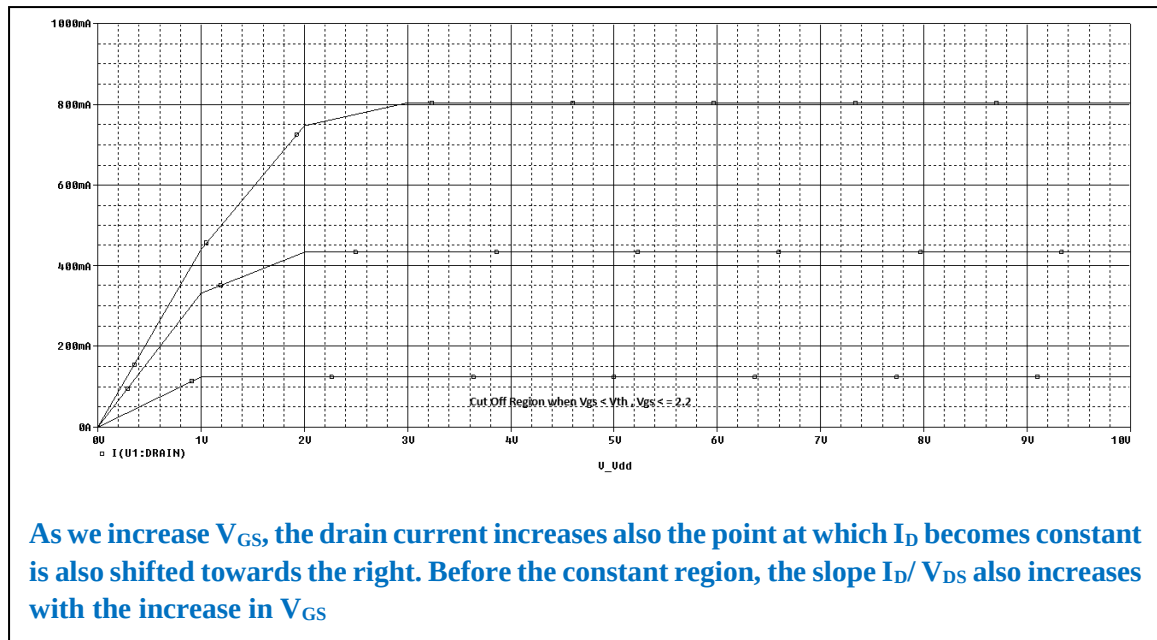

Task 5: To determine trans-conductance g_m of MOSFET 2N7000

The trans-conductance g_m describes the effect the gate has on the conductivity of the MOSFET at a certain operating point. The trans-conductance of a MOSFET in the linear region is given as:

$$g_m = \left. \frac{\partial I_D}{\partial V_{GS}} \right|_{V_{DS}=\text{constant}} = \left. \frac{\Delta I_D}{\Delta V_{GS}} \right|_{V_{DS}=\text{constant}}$$

1. From the I_D - V_{GS} curve of Task 2, determine trans-conductance. Use cursors to measure the small change in current for small change in voltage (around 100-200mV).

Table 2: Data collection to determine trans-conductance

Change in current: ΔI_D	31.965mA
Change in current: ΔV_{GS}	100mV (3.6 – 3.5)
Trans-conductance: g_m	0.319

Task 6: To obtain the threshold voltage of MOSFET 2N7000 through hardware implementation.

1. Using a 10 k Ω potentiometer, as indicated by the circuit below, determine the MOSFET's threshold voltage, V_{TH} , by monitoring the drain voltage V_{DS} , as you vary the gate voltage V_G , using the potentiometer. It is recommended to adjust the threshold voltage to be that voltage for which the drain current reaches 0.1 mA.
2. Measure the actual resistance of drain resistor R_D using a digital multimeter and record the reading.

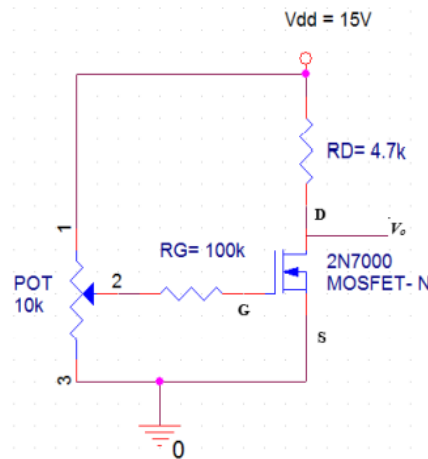


Figure 3: Common Source 2N7000 MOSFET Configuration

3. Record your readings in the below table.

Table 3: MOSFET Input Characteristic Measurement

Drain Resistor: R_D	4.7k
Drain Current: I_D	101uA
Gate Voltage: V_{GS}	1.4 V
Threshold Voltage: V_{TH}	1.41 V
Drain Voltage: V_{DS}	14.79 V

4. According to the readings in Table 3, what is the mode of the operation of the MOSFET? Justify it through the values of V_{TH} , V_{GS} and V_{DS} .

$V_{DS} < V_{GS} - V_{TH}$
14.79 < 0 (not triode region)
 $V_{DS} > V_{GS} - V_{TH}$ (Saturation region)
14.79 > 0
And
 $V_{GS} \geq V_{TH}$
1.4 ≥ 1.41

Task 7: To investigate the effect of gate voltage on the drain characteristics of MOSFET 2N7000 by hardware implementation.

The drain current of the mosfet in the saturation region can be calculated by the equation given below.

Where, K is known as the process transconductance parameter and equals to:

$$K = \mu_n C_{ox} \frac{W}{L}$$

- Using the same circuit as shown in Figure 3, increase the gate voltage so that it is 0.25 volts above threshold. Calculate the drain current by measuring the voltage drop across the drain resistor R_D . Note down the calculated values in Table 04.

2. Now determine the value of K using the above equations.

$$K = 0.066$$

3. Using the values of V_{TH} and K determined above for your transistor, calculate the value of V_{GS} required for a drain current $I_D = 2\text{mA}$ using the given formula. Use a source resistor $R_S = 2.2\text{ k}\Omega$ to find values of R_{G1} and R_{G2} required to produce this gate-source voltage (since there is a sizeable leakage current with this set-up recommended value of R_{G1} is $20\text{ k}\Omega$) while using the below circuit. Show calculation.

$$I_D = \frac{K}{2} (V_{GS} - V_{TH})^2$$

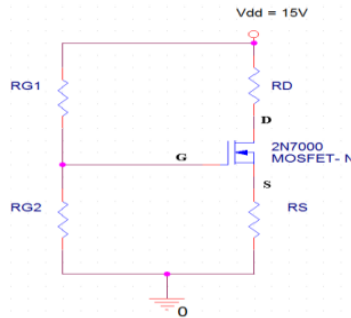


Figure 4: Voltage Divider Bias 2N7000 MOSFET Configuration

4. Construct the bias circuit above using the available resistor values that best match your design (i.e., those that give the closest value of V_{GS})

$$2 \times 10^{-3} = \frac{0.066}{2} (V_{GS} - 1.4)^2$$

$$V_{GS} = 1.646\text{V}$$

$$V_{GS} = V_G - V_S$$

$$1.646 = V_G - V_S$$

$$V_S = I_D R_S$$

$$V_S = (2 \times 10^{-3}) (2.2 \times 10^3)$$

$$V_S = 4.4\text{V}$$

$$V_{GS} = V_G - V_S$$

$$1.646 = V_G - 4.4$$

$$V_G = 6.046\text{V}$$

$$-15 + I_D R_D + V_{DS} + I_D R_S = 0$$

$$-15 + (2\text{mA})(4.7\text{k}) + V_{DS} + (2\text{mA})(2.2\text{k}) = 0$$

$$V_{DS} = 1.2\text{V}$$

$$V_G = V_{DD} \frac{R_{G2}}{R_{G1} + R_{G2}}$$

$$6.046 = \frac{(15) R_{G2}}{20 \times 10^3 + R_{G2}}$$

$$R_{G2} = 13.504\text{ k}\Omega$$

5. Measure the resistances, gate and drain voltages, and the drain current and fill them in the below table.

Table 4: Data collection

	Calculated Results	Measured Results
V_{GS}	1.646V	1.61V
V_{DS}	1.2V	1.81V
I_D	2mA	1.55mA
R_{G1}, R_{G2}, R_S	$R_S = 2.2\text{ k}\Omega, R_{G1} = 20\text{ k}\Omega, R_{G2} = 1350.4\Omega$	$R_S = 2.2\text{ k}\Omega, R_{G1} = 20\text{ k}\Omega, R_{G2} = 1350.4\Omega$

6. Now, calculate the transconductance, g_m of given transistor under biased conditions using the below formula:

$$g_m = \frac{2I_D}{(V_{GS} - V_{TH})}$$

$g_m = \frac{2 \times 1.55 \times 10^{-3}}{1.61 - 1.3} = 0.01$

$g_m =$

Task 8: To determine the channel resistance r_d of MOSFET 2N7000

In triode region, you can see that the slope of I_D - V_{DS} curve changes with change in V_{GS} . This slope determines channel resistance r_d . It is the ratio of small change in drain to source voltage (ΔV_{DS}) to the corresponding change in drain current (ΔI_D) for a constant V_{GS} .

$$r_d = \left. \frac{\partial V_{DS}}{\partial I_D} \right|_{V_{GS}=\text{constant}} = \left. \frac{\Delta V_{DS}}{\Delta I_D} \right|_{V_{GS}=\text{constant}}$$

- Find this channel resistance for different values of V_{GS} , from the characteristic curves of Task 4. Use cursors and measure it at the center of triode region in each curve. Let, the small change in voltage be 0.2V.
- Fill in Table 5.

Table 5: Data collection for determination of channel resistance

V_{GS}	3V	4V	5V
Change in current: ΔI_D	24.66 mA	50.25 mA	55.249 mA
Change in current: ΔV_{DS}	0.2V	0.2V	0.2V
Channel resistance: r_d	8.11 Ω	3.98 Ω	3.61 Ω

- Analyze the impact of gate-to-source voltage on this channel resistance in triode region. What will be the value of this channel resistance in saturation region for the ideal behavior of MOSFETs as obtained in simulation?

When the value of V_{GS} gets higher. In triode region, the channel resistance varies with the V_{GS} , as V_{GS} increases the channel becomes more conductive reducing r_d . In saturation region, the channel resistance is considered zero for the ideal diode.

Assessment Rubric
Lab 08
MOSFET Characteristics

Name: Syed M. Asad Ali Hiba Aiman Ali, M. Asad Siddiqui	Student ID: sa09475, ha09269, ms09200
--	--

Points Distribution

Task No.	LR1/2 Circuit /Simulation 24	LR 4 Data Collection 22	LR 5 Plots 20	LR 6 Calculation 10	LR 10 Analysis 20
Task 1	-	-	-	-	/4
Task 2	/4	/2	/4	-	-
Task 3	/6	/4	/8	-	/4
Task 4	/6	-	/8	-	/6
Task 5	-	/4	-	/2	-
Task 6	/4	/4	-	/2	/2
Task 7	/4	/4	-	/4	-
Task 8	-	/4	-	/2	/4
CLO Mapped	CLO 3	CLO 1	CLO 3	CLO 1	CLO 1
	/24	/22	/20	/10	/20

Affective Domain Rubric		Points	CLO Mapped
AR 4	Report Submission	/4	CLO 4

CLO – (LDL)	Total Points	Points Obtained
CLO1– (Psy-3)	52	
CLO3 – (Psy-4)	44	
CLO4 – (Aff-3)	04	
Total	100	

For description of different levels of the mapped rubrics, please refer the provided Lab Evaluation Assessment Rubrics and Affective Domain Assessment Rubrics.