

Q.1) For series and parallel RLC circuits the conditions for over-damped, under-damped and critically damped circuits are:


Overdamped: $R^2 > 4L/C$

Underdamped: $R^2 < 4L/C$


critically damped: $R^2 = 4L/C$

Series RLC circuit


critically damped:

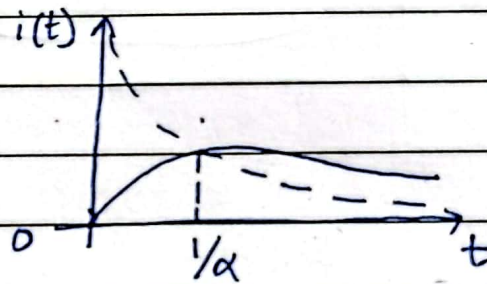

Over damped:

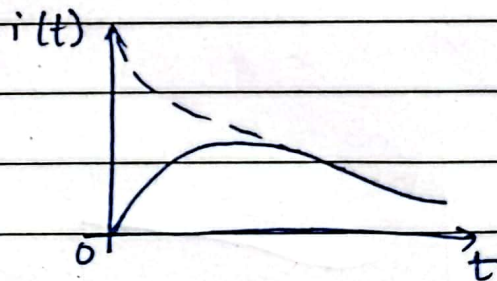


Under damped:

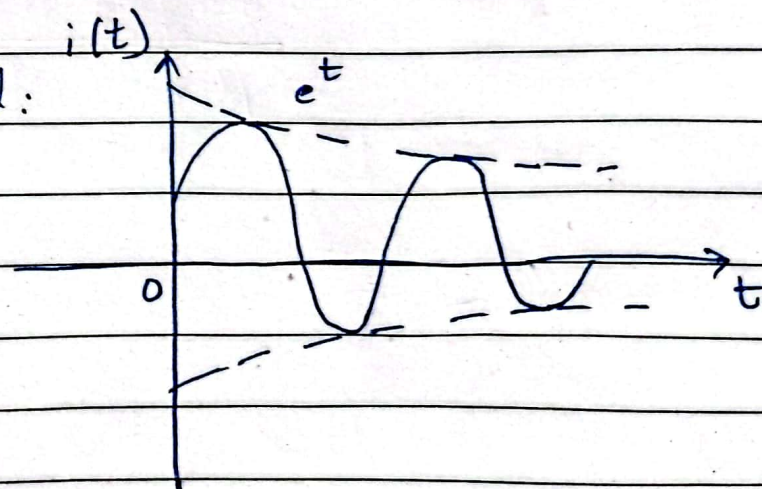


Parallel RLC Circuit:

Under
~~Critically~~ damped:

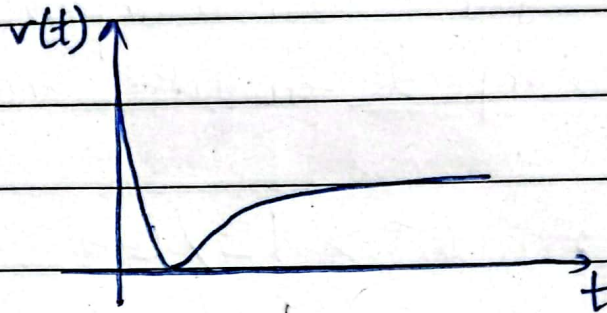


Overdamped:

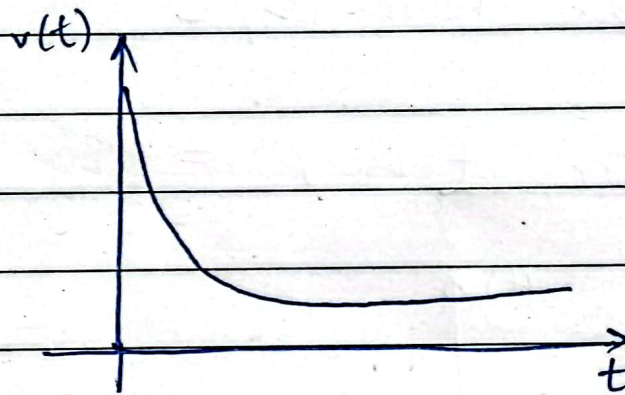

~~Underdamped~~:

Critically damped:

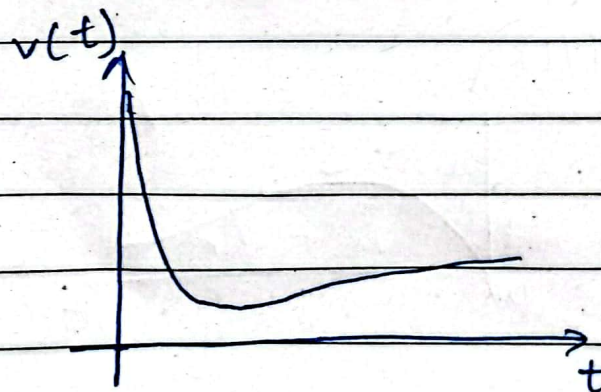

$$Q.2) \quad X_C = \frac{-j}{2\pi f C}, \quad X_L = j 2\pi f L$$

$$|Z| = \sqrt{R^2 + (X_L - X_C)^2}, \quad \phi = \tan^{-1} \left(\frac{X_L - X_C}{R} \right)$$

$$R = 1k\Omega, \quad L = 10mH, \quad C = 10nF$$

At $f = 8k Hz$:

$$X_C = \frac{-j}{2\pi(8k)(10n)} = \boxed{1989.4\Omega}, \quad X_L = j 2\pi(8k)(10m) = \boxed{502.7\Omega}$$

$$\Rightarrow X_L - X_C = -1486.7$$

$$|Z| = \sqrt{(1k)^2 + (-1486.7)^2} = \boxed{1791.8\Omega}$$

$$\phi = \tan^{-1} \left(\frac{-1486.7}{1000} \right) = \boxed{-56.07^\circ}$$

At $f = 12k Hz$:

$$X_C = \frac{-j}{2\pi(12k)(10n)} = \boxed{1326.3\Omega}, \quad X_L = j 2\pi(12k)(10m) = \boxed{753.98\Omega}$$

$$X_L - X_C = -572.32$$

$$|Z| = \sqrt{(1k)^2 + (-572.32)^2} = \boxed{1152.2\Omega}$$

$$\phi = \tan^{-1} \left(\frac{572.32}{1000} \right) = \boxed{-29.78^\circ}$$

At $f = 16 \text{ kHz}$:

$$X_C = \frac{-j}{2\pi(16\text{k})(10\text{n})} = \boxed{994.7 \Omega}, \quad X_L = 2\pi(16\text{k})(10\text{m}) = \boxed{1005.3 \Omega}$$

$$X_L - X_C = 10.6$$

$$|Z| = \sqrt{(1000)^2 + (10.6)^2} = \boxed{1000.06 \Omega}$$

$$\phi = \tan^{-1}\left(\frac{10.6}{1000}\right) = \boxed{0.607^\circ}$$

At $f = 20 \text{ kHz}$:

$$X_C = \frac{-j}{2\pi(20\text{k})(10\text{n})} = \boxed{795.78 \Omega}, \quad X_L = 2\pi(20\text{k})(10\text{m}) = \boxed{1256.6 \Omega}$$

$$X_L - X_C = 460.86$$

$$|Z| = \sqrt{(1\text{k})^2 + (460.86)^2} = \boxed{1101.95 \Omega}$$

$$\phi = \tan^{-1}\left(\frac{460.86}{1000}\right) = \boxed{24.74^\circ}$$

At $f = 24 \text{ kHz}$:

$$X_C = \frac{-j}{2\pi(24\text{k})(10\text{n})} = \boxed{663.15 \Omega}, \quad X_L = 2\pi(24\text{k})(10\text{m}) = \boxed{1508 \Omega}$$

$$X_L - X_C = 814.8 \Omega$$

$$|Z| = \sqrt{(1\text{k})^2 + (814.8)^2} = \boxed{1309.1 \Omega}$$

$$\phi = \tan^{-1}\left(\frac{814.8}{1000}\right) = \boxed{39.2^\circ}$$

Date: _____

At $f = 30\text{K Hz}$:

$$X_C = \frac{-j}{2\pi(30\text{K})(10\text{n})} = 530.5 \Omega \quad X_L = 2\pi(30\text{K})(10\text{m}) = 1885 \Omega$$

$$X_L - X_C = 1354.46 \Omega$$

$$|Z| = \sqrt{(1000)^2 + (1354.46)^2} = 1683.6 \Omega$$

$$\phi = \tan^{-1} \left(\frac{1354.46}{1000} \right) = 53.56^\circ$$

	Freq (Hz)	X_C	X_L	$Z \angle \phi$
	8k	1989.4 Ω	502.7 Ω	1791.8 $\angle -56.07^\circ$
	12k	1326.3 Ω	753.98 Ω	1152.2 $\angle -29.78^\circ$
	16k	994.7 Ω	1005.3 Ω	1000.06 $\angle 0.607^\circ$
	20k	795.78 Ω	1256.6 Ω	1101.1 $\angle 24.74^\circ$
	24k	663.15 Ω	1508 Ω	1309.1 $\angle 39.2^\circ$
	30k	530.5 Ω	1885 Ω	1683.6 $\angle 53.56^\circ$